
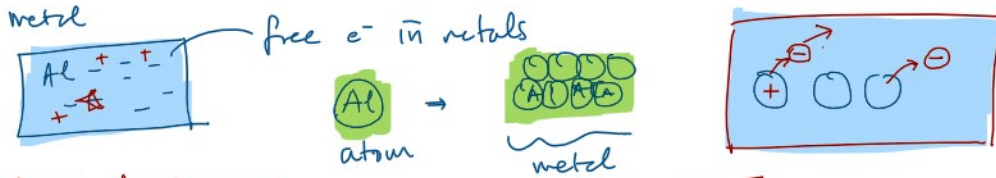


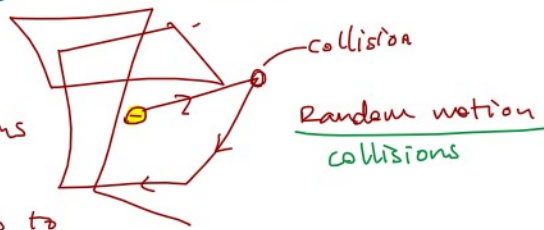
Chapter 25: Current Resistance & Electromotive Force
 upto now electrostatics $\vec{E}$, $\vec{F}$, V , C ...
 after ch 25 Electrodynamics charges are moving.



- abundance of charges (-) free
- free e- collide with other e-, and atoms
- electrostatic = time average of an e-, e- seems to stay.



What if we apply $\vec{E}$ in the metal.

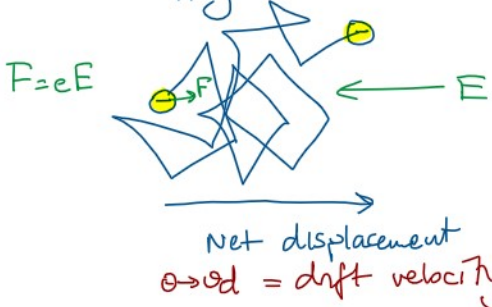

$\vec{E}$ field drift (suriklane) e- in the metal.

collisions + eE force



$$v_d \sim \text{mm/s} \sim 10^{-3} \text{ m/s} \ll 10^6 \text{ m/s}$$



current is defined wrt. $\oplus$ charge definitions.


$$\text{current } I \equiv \frac{Q}{t} = \frac{\Delta Q}{\Delta t} = \left[\frac{\text{Coulomb}}{\text{sec}} = \text{Ampere} \right] ; \frac{C}{s} = A$$

one of SI units

$$\text{Phys I} \Rightarrow \frac{\text{kg}}{\text{m} \cdot \text{s}}$$

$$\text{Phys II } A \sim \frac{\text{charge}}{\text{time}} [C = A \cdot s]$$

wire

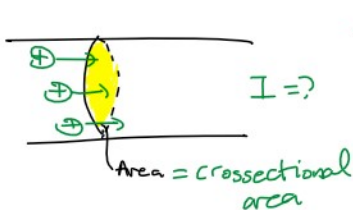

$$I = \frac{Q}{t} ; I \uparrow$$

$$\frac{q}{t} = \text{Ampere}$$

$$\frac{\mu C}{\text{ms}} = \text{mA}$$

$$\frac{\Delta Q}{\Delta t} = I$$

$$\Delta Q = q_e (\text{number of charges})$$


$$\hookrightarrow (1.6 \times 10^{-19} \text{ C})$$

number of charges depends on the metal

$$n = \frac{\text{number of charge}}{\text{Volume}} = \left[\frac{\text{number}}{\text{m}^3} \right]$$



$AL = \text{volume}$

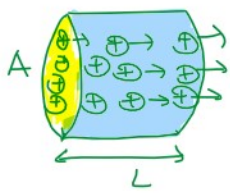

number of charges

$n \text{ volume} = nAL$

$$\frac{q_e(nAL)}{\Delta t} = \frac{\Delta Q}{\Delta t} = I$$

$$I = \frac{q_e n A L}{\Delta t}$$

velocity drift

$$L = v_d \Delta t$$

$$I = q_e n A v_d$$

$$q_e = 1.6 \times 10^{-19} \text{ C}$$



$I \propto A$

$$J \equiv \text{current density} = \frac{I}{A} = q_e n v_d = \left[\frac{A}{m^2} \right]$$

$$\left[\frac{C}{m^3} \frac{1}{m} \frac{m}{s} = \frac{A}{m^2} \right]$$

ex) Cu wire diameter of 1.02 mm $I = 1.67 \text{ A}$

free e- density $n = 8.5 \times 10^{28} \frac{1}{m^3}$ $J = ?$ $v_d = ?$

$$J = \frac{I}{A} = \frac{1.67 \text{ A}}{\pi \left(\frac{1.02 \times 10^{-3} \text{ m}}{2} \right)^2} = 2 \times 10^6 \text{ A/m}^2$$


$v_d = ?$

$$I = q_e n A v_d$$

$$J = q_e n v_d$$

$$v_d = 0.15 \text{ mm/s} = 1.5 \times 10^{-4} \text{ m/s} \text{ (very small)}$$

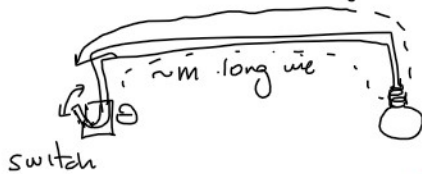
Q) How come turning the lights on/off is much faster than v_d ?



switch

How are e- everywhere
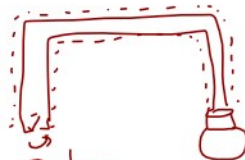
$$\frac{1 \text{ m}}{v_d} \sim \frac{1 \text{ m}}{0.1 \text{ mm/s}} \sim 10^3 \text{ s} \sim 20 \text{ minutes}$$



$$v \sim 10^6 \text{ m/s}$$

one e- to jump from left to right on the switch is enough to turn on the light.

Resistivity (Divera)


conductivity

$$J = \sigma E$$

$$J = E$$

resistivity

$$\rho \sigma = 1$$

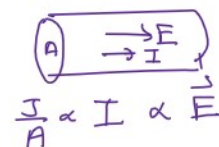

$$\frac{I}{A} \propto I \propto E$$

$$J = \sigma E$$

$$J = \sigma E$$

$$J = \frac{E}{\rho}$$

$$\rho J = E$$

resistivity

$$\rho \sigma = 1$$

$$\frac{J}{A} \propto I \propto E$$

Ohm's Law

$$J = \sigma E$$

$$\frac{A}{m^2} = \sigma \frac{V}{m}$$


$$\int E dr = \Delta V$$

$$E = \frac{\text{volt}}{\text{meter}} = \frac{V}{m}$$

$$\left[\rho = \frac{V_m}{A} \right]$$

$$\left[\sigma = \frac{A}{V_m} \right] \Rightarrow$$
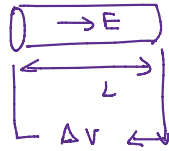
$$\frac{I}{A} = J = \frac{E}{\rho} = \frac{\Delta V}{\rho L}$$



$$\Delta V = E L$$

$$\frac{\Delta V}{\rho L} = \frac{I}{A}$$

$$\Delta V = \left(\rho \frac{L}{A} \right) I = R I$$

Ohm's Law

$$\Delta V = I R$$

$$R \equiv \text{resistance} = \rho \frac{L}{A}$$

ρ = resistivity

$$R \equiv [R] = \text{ohm}$$


$$\rho = \frac{R A}{L} = \left[\frac{\Omega m^2}{m} \right]$$

Table 25.1 Resistivities at Room Temperature (20°C)

Substance	ρ ($\Omega \cdot m$)	Substance	ρ ($\Omega \cdot m$)
Conductors		Semiconductors	
Metals		Pure carbon (graphite)	3.5×10^{-5}
Silver	1.47×10^{-8}	Pure germanium	0.60
Copper	1.72×10^{-8}	Pure silicon	2300
Gold	2.44×10^{-8}		
Aluminum	2.75×10^{-8}	Insulators	
Tungsten	5.25×10^{-8}	Amber	5×10^{14}
Steel	20×10^{-8}	Glass	$10^{10} - 10^{14}$
Lead	22×10^{-8}	Lucite	$> 10^{13}$
Mercury	95×10^{-8}	Mica	$10^{11} - 10^{15}$
Alloys		Quartz (fused)	75×10^{16}
Manganin (Cu 84%, Mn 12%, Ni 4%)	44×10^{-8}	Sulfur	10^{15}
Constantan (Cu 60%, Ni 40%)	49×10^{-8}	Teflon	$> 10^{13}$
Nichrome	100×10^{-8}	Wood	$10^8 - 10^{11}$

$$\rho \sim 10^{-8} \text{ to } 10^{24}$$

$$J = \frac{I}{A} = \frac{E}{\rho}$$

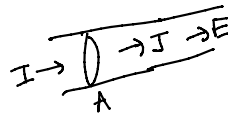

$$R = \rho \frac{L}{A}$$

$$[\Omega m] = \rho$$


$$\frac{I}{A} = J = \frac{E}{\rho} \quad \text{Ohm's Law}$$

$$E = \frac{\Delta V}{L}$$

$$\Rightarrow \frac{I}{A} = \frac{\Delta V}{L} \frac{1}{\rho} \Rightarrow \Delta V = \underbrace{\rho \frac{L}{A}}_R I \Rightarrow \Delta V = I R \quad \text{Ohm's Law}$$

R = resistance (diring)

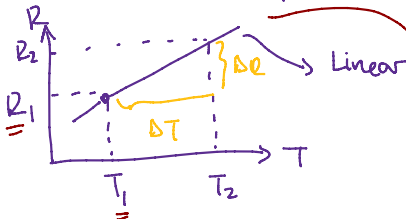$\Rightarrow$ Resistance is Temperature dependent




$$\text{slope} = \frac{\Delta R}{\Delta T} = \frac{R_2 - R_1}{T_2 - T_1} = \alpha$$

$$R_2 = \alpha (T_2 - T_1) + R_1$$

$$R_1, T_1 \checkmark @ T_2 \quad R_2?$$



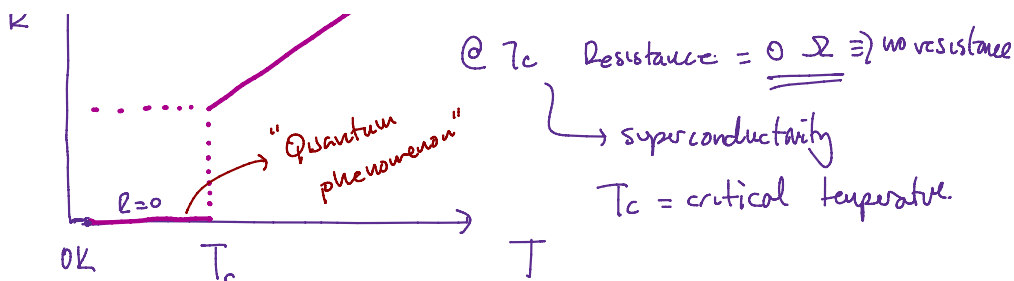
@ T_c Resistance = 0 Ω $\Rightarrow$ no resistance



@ superconductivity

$$\underline{T < T_c}$$

$$T_c \sim 4K$$

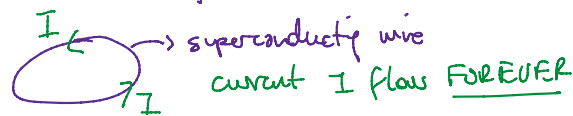

$$T_c \sim 140K$$

idea is to create materials that would be superconducting closer to room temperature.


MRI

(magnetic resonance imaging) = "EMAR"

ex) $\alpha = 0.00393 \frac{1}{^\circ C}$ $R @ 25^\circ C = 1.05 \Omega$

$R @ 0^\circ C = ?$

$R @ 100^\circ C = ?$

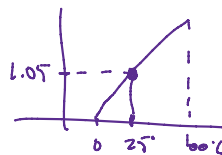

$$R_2 = R_1 + \alpha (T_2 - T_1)$$

$$R_2(0^\circ C) = 1.05 + 0.00393(0 - 25) \quad \left\{ \quad R_2(100^\circ C) = 1.05 + 0.00393(100 - 25) \right.$$


$$= 0.97 \Omega \quad \quad \quad = 1.38 \Omega$$

ex) $A = 8.2 \times 10^{-7} m^2$

$L = 50m$

$I = 1.67 A$

$\rho = 1.72 \times 10^{-8} \Omega m$

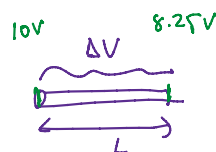

a) ΔV between two ends of wire?

$$\Delta V = I R = I \rho \frac{L}{A} = 1.75 V$$

b) E field in the wire?

$$E L = \Delta V \Rightarrow E = \frac{\Delta V}{L} = \frac{1.75}{50} \frac{V}{m} = 0.035 \frac{V}{m} = 0.035 \frac{N}{C}$$


unit of E

c) R of wire?

$$\rho \frac{L}{A} = R = 1.05 \Omega$$

Electromotor Force (EMF) $\equiv$ Battery

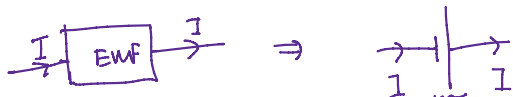EMF makes current move from + side to - side



EMF source = Battery (pi)

EMF source

EMF (Volts) ; "chemical reactions inside the battery gives out the energy to create current flow"


Battery $\equiv$ active research area $\rightarrow$ smaller
 $\rightarrow$ more powerful
 $\rightarrow$ long lasting
 $\rightarrow$ short recharge time
 $\rightarrow$ lower internal resistance

All of the batteries have internal resistance

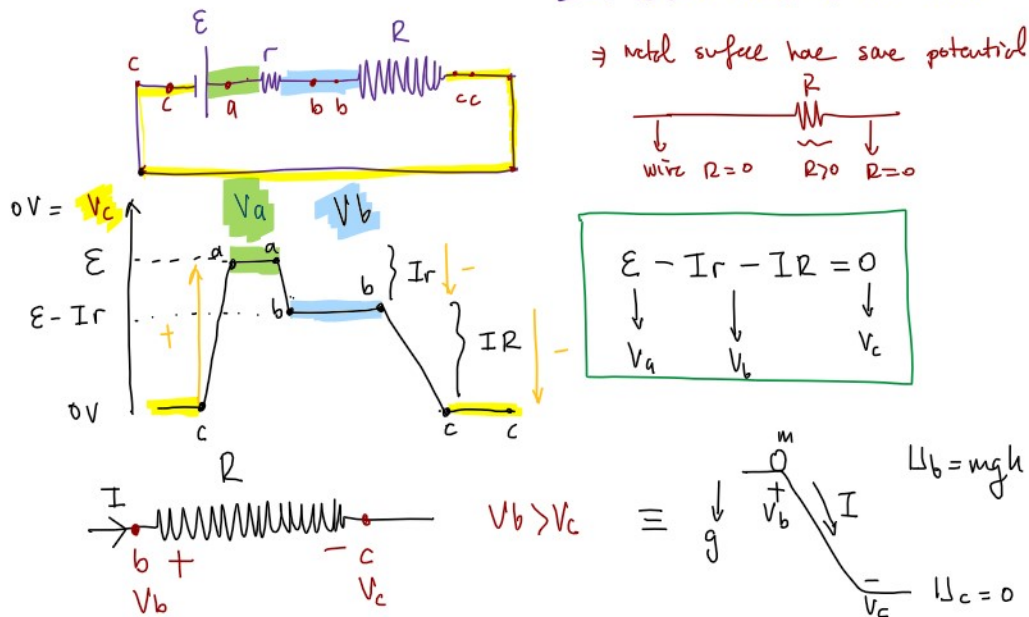1.5V $\Rightarrow \frac{1}{r} \mathcal{E} = \Delta V$
 $r = \text{internal resistance}$

Ideal battery $r = 0 \Omega$

$\rightarrow$ we will use it in our course.



current I flows towards lower potential

if $\mathcal{E} = 12V$
 $Ir = 4V$
 $IR = 8V$

$\mathcal{E} - Ir - IR = 0 \rightarrow I = \frac{\mathcal{E}}{r+R} = \frac{12}{2+4} = 2A$
 $12 - 4 - 8 = 0$
 $r = 2\Omega \quad R = 4\Omega$

Power & Energy $\Delta V = IR$

$\rightarrow P = \frac{\text{Energy}}{\text{time}} = \left[\frac{J}{s} = \text{watts} \right]$


$\Delta V = V_f - V_i = V_- - V_+ < 0$

$[V = A\Omega]$
 $\Delta V = IR$


$P = \frac{\Delta U}{t} = \frac{q \Delta V}{t} = \frac{q}{t} \Delta V = I \Delta V = \text{Power}$

$[A \cdot V = \text{watts} = \frac{J}{s}]$

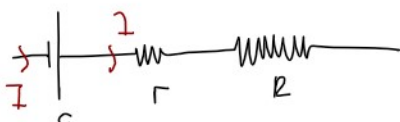$P = I \Delta V = I (IR) = I^2 R = \left(\frac{\Delta V}{R} \right) \Delta V = \frac{\Delta V^2}{R}$



Electric bills (kW sa)
 paying (kW hr)

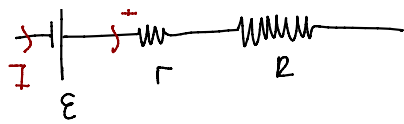

creates power = consume power

$$I\mathcal{E} = I^2 r + I^2 R$$

Electric power (kW or J/s)
paying
energy = power × time
 $E = P t$
 $J = W s$

$$1 = \text{kW hr}$$

$$= 1000 \text{ W } 3600 \text{ s}$$

$$\text{energy} = 3.6 \times 10^6 \text{ J}$$

If we run an oven 240V, $I = 20 \text{ A}$
for 4 hrs. power consumed?

$$P = I \Delta V = (240 \text{ V})(20 \text{ A}) = 4800 \text{ Watt} = 4.8 \text{ kW}$$

$$\text{Energy consumed } P t = (4.8 \text{ kW})(4 \text{ hrs}) = 19.2 \text{ kW hr}$$

⇒

Heat up the room with resistive heaters ≡ "WFO"

$$\Rightarrow \text{Power WFO} = 2000 \text{ watts}$$

$$\Rightarrow \text{cold winter month} \Rightarrow \text{one day } \underline{6 \text{ hrs}} \Rightarrow \text{ON OFF } \underline{3 \text{ hrs per day}}$$

$$30 \text{ days} \times 3 \text{ hrs} = 90 \text{ hrs/month} \approx 100 \text{ hrs/month}$$

$$2000 \text{ W} \times 100 = 200 \text{ kW hr} \equiv \underline{\underline{520 \text{ TL}}}$$

2.6 TL

⇒

End of CH 25

$$\hookrightarrow I = \frac{q}{t} \Rightarrow$$

$$n q v_d A = I$$

$$J = \frac{I}{A} = \frac{E}{P}$$


$$R = \rho \frac{L}{A} ; \underline{\underline{\Delta V = IR}}$$

CH 26

DC circuits

$$\Delta V = IR ;$$

Resistors in series connection

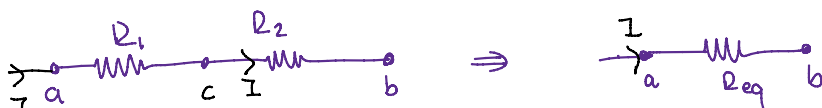

$$V_{ac} + V_{cb} =$$

$$V_{ab}$$

$$IR_1 + IR_2 =$$

$$I R_{eq}$$


$$\boxed{R_{eq} = R_1 + R_2}$$

$$\text{---} \text{---} \text{---} \dots \text{---} \Rightarrow \boxed{R_{eq} = R_1 + R_2 + \dots + R_N \text{ SERIES.}}$$

Resistors in parallel connection



$$R_{eq}$$

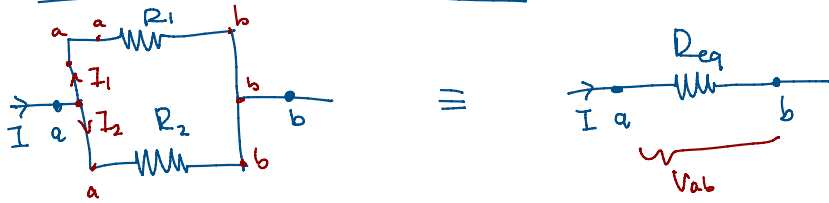


V_{ab} same for R_1 & R_2

$$I_1 + I_2 = I$$

$$\frac{V_{ab}}{R_1} + \frac{V_{ab}}{R_2} = \frac{V_{ab}}{R_{eq}}$$

$$\left[\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_{eq}} \right] \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$
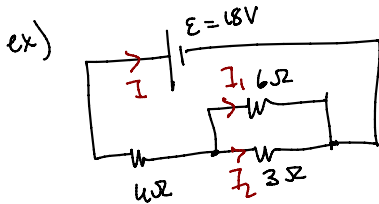
$$\left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_N} \right]^{-1} = R_{eq}$$



$R_{eq}?$

$I=?$


$I_1=?$

$I_2=?$

$V_{6\Omega}=?$


$P_{6\Omega}=?$

power of the circuit?

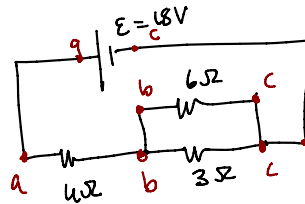


$$4 + (6 \parallel 3)$$
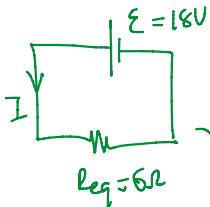
$$4 + \frac{6(3)}{6+3} = 6\Omega = R_{eq}$$



$$I = \frac{18}{6} = 3A$$

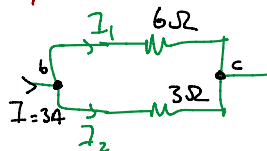


$$V_{6\Omega} = I_1 6\Omega = 1(6) = 6V$$

$$V_{3\Omega} = I_2 3\Omega = 2(3) = 6V$$

$$V_{4\Omega} = I(4\Omega) = 3(4) = 12V$$

$$\mathcal{E} = 18V$$

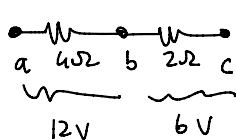

$$V_{bc} = V_{bc} = V_{6\Omega}$$

$$I_1 6 = I_2 3$$

$$I_1 + I_2 = 3A$$

$$I_1 + 2I_1 = 3A$$


$$I_1 = 1A \quad I_2 = 2A$$

$$P_{6\Omega} = I^2 R = 1^2(6) = 6W$$

$$P_{3\Omega} = I^2 R = 2^2(3) = 12W$$

$$P_{4\Omega} = I^2 R = 3^2(4) = 36W$$

$$+ \quad 54W$$

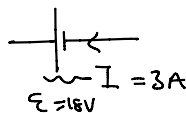


$$P_{\mathcal{E}} = I \mathcal{E} = 3(18) = 54W$$



$$= 54W$$

$$\frac{+}{54 \text{ W consumed}} = 54 \text{ W created}$$

{ 54 W = power of circuit }

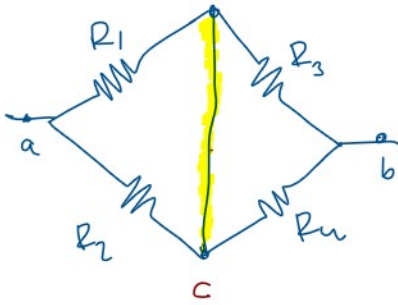


$R_{ab} = ?$

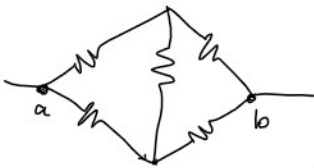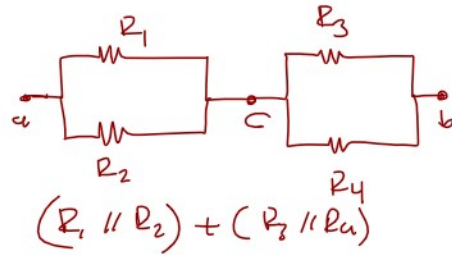

$R_{ab} = ?$ neither series nor parallel !!


KIRCHHOFF RULES (LAWS)

• Node (Điểm)

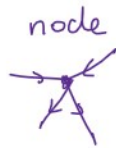


we use Kirchhoff to calculate complicated circuits.

• LOOP (Dòng)

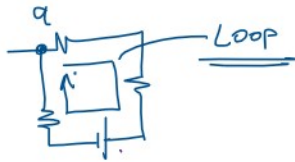

KIRCHHOFF CURRENT LAW (KCL)

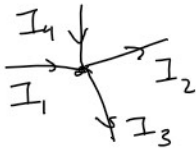The INCOMING and OUTGOING currents are EQUAL to each other at the NODE.



$$\sum I_{in} = \sum I_{out}$$

$$I_1 + I_4 = I_2 + I_3$$

KIRCHHOFF VOLTAGE LAW (KVL)

→ the sum of all potential differences around any loop is zero




$$\Delta V_{a \rightarrow a} = 0 = V_a - V_a$$

HOW TO CALCULATE POTENTIAL DIFFERENCE

→ LOOP





Resistors

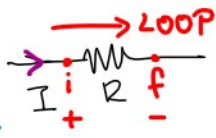


$$\Delta V = V_f - V_i < 0$$

$$\Delta V = -IR$$

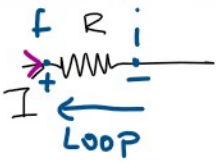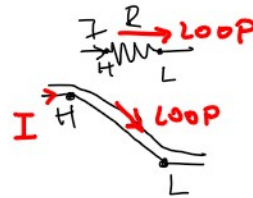


$$\Delta V = V_f - V_i > 0$$

$$\Delta V = +IR$$

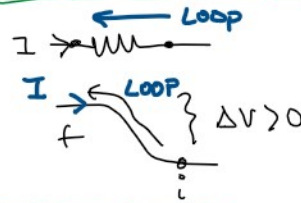


Battery

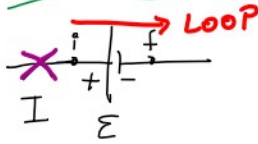

$$\Delta V = V_f - V_i < 0$$

$$\Delta V = -\epsilon$$

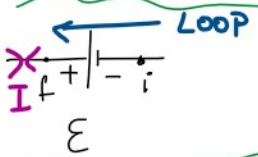


$$\Delta V = V_f - V_i > 0$$

$$\Delta V = +\epsilon$$


Direction of current
does NOT matter!!
for batteries

Capacitors

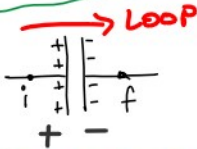

$$\Delta V = V_f - V_i < 0$$

$$\Delta V = -\frac{Q}{C}$$

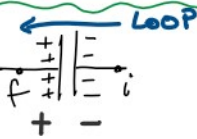


$$\Delta V = V_f - V_i > 0$$


$$\Delta V = +\frac{Q}{C}$$

Direction of
current does NOT
matter. FIND + charges
SIDE, that side has
HIGHER Potential

ex)

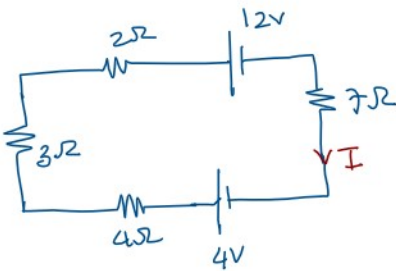

I = ?

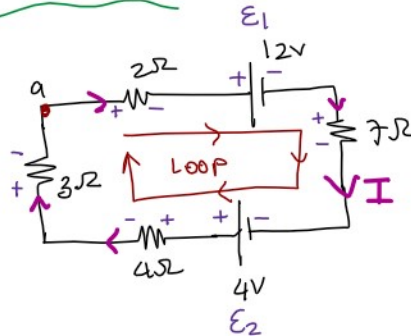

KVR

$$-V_{2\Omega} - \epsilon_1 - V_{7\Omega} + \epsilon_2 - V_{4\Omega} - V_{3\Omega} = 0$$


$$-2I - 12 - 7I + 4 - 4I - 3I = 0$$

$$-16I = 8$$

$$I = -\frac{1}{2}A = -0.5A \quad \checkmark \quad \text{DONE!!}$$

$$\checkmark I = -0.5A \Rightarrow \uparrow I = 0.5A$$

ex)

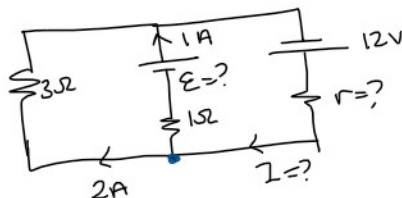


$$I = ?$$


$$r = ?$$

$$\epsilon = ?$$

(KCL)

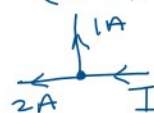


$$I = 2 + 1 = 3A \quad \checkmark$$

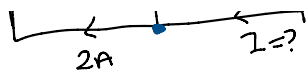

$\Sigma = ?$

$$I = 2 + 1 = 3A \quad \checkmark$$

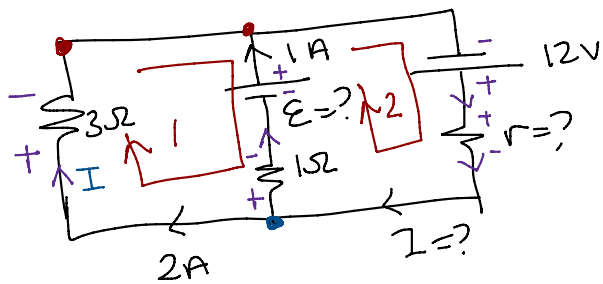

$$1) -\mathcal{E} + (1A)(1\Omega) - (2A)(3\Omega) = 0$$

$$-\mathcal{E} + 1 - 6 = 0$$


$$\mathcal{E} = -5V$$

$$2) +12V - Ir - 1A(1\Omega) + \mathcal{E} = 0$$

$$12 - 3r - 1 - 5 = 0$$

$$3r = 6 \Rightarrow r = 2\Omega$$

ex)

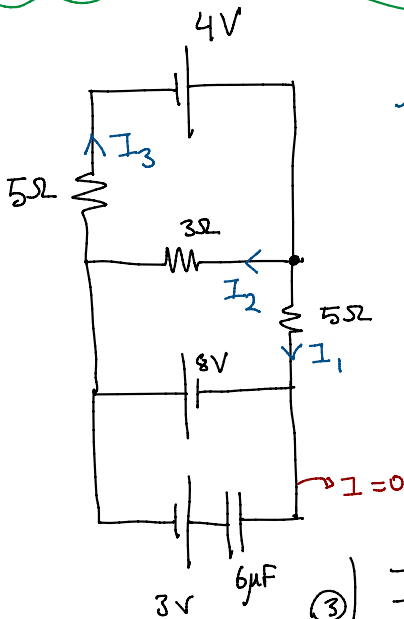


In this circuit
we wait long enough for the capacitor to
charged fully.

$$I_1 = ?$$

$$I_2 = ?$$



$$I_3 = ?$$

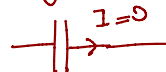

FULLY charged } I on capacitor = 2ERR!

KCL (Law)

$$3) I_3 = I_2 + I_1$$

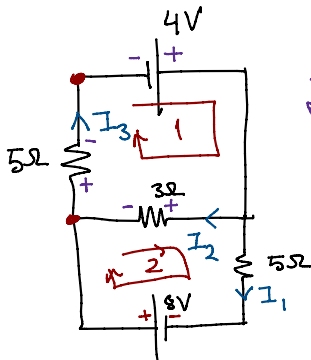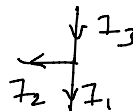

$$1) 4 - 3I_2 - 5I_3 = 0 \Rightarrow 4 - 3I_2 - 5I_2 - 5I_1 = 0$$

$$2) 3I_2 - 5I_1 + 8 = 0$$

$$4 - 8I_2 - 5I_1 = 0 \quad ①$$

②

$$4 = 8I_2 + 5I_1$$

$$-1 \quad (8 = -8I_2 + 5I_1)$$

$$-4 = 11I_2 \Rightarrow I_2 = -4/11 A$$

$$4 = 8\left(\frac{-4}{11}\right) + 5I_1$$


$$\frac{44 + 32}{11} = 5I_1$$

$$I_1 = \frac{76}{55} A$$


??

$$I_3 = I_1 + I_2 = \frac{-4}{11} + \frac{76}{55} = \frac{56}{55} A$$


b) charge on the capacitor?

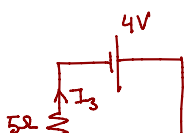

$$-8 + V_c - 3 = 0$$

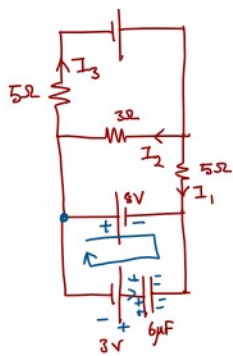


b) charge on the capacitor

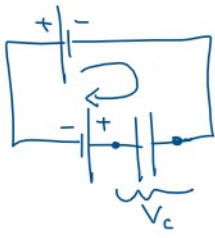

$$8 + 3 - V_c = 0$$

$$V_c = 11V \Rightarrow Q = CV = (6\mu F) 11V$$

$$Q = 66\mu C$$



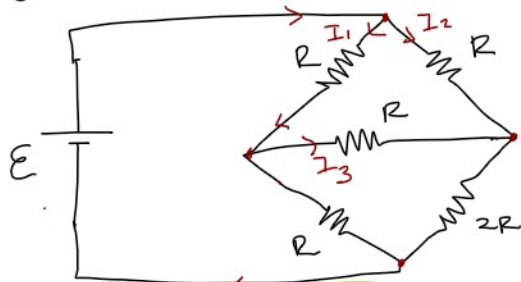


$$R = 1\Omega$$

$$\mathcal{E} = 13V$$

$$I_1, I_2, I_3?$$

R_{eq} of the circuit?

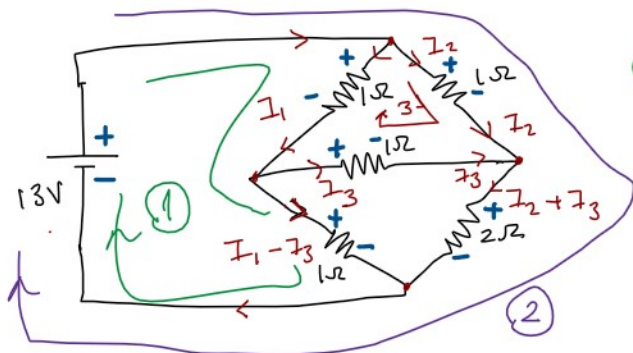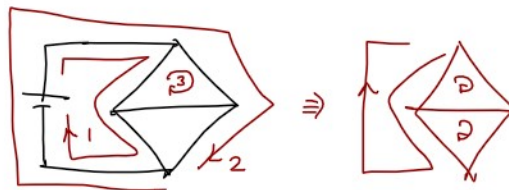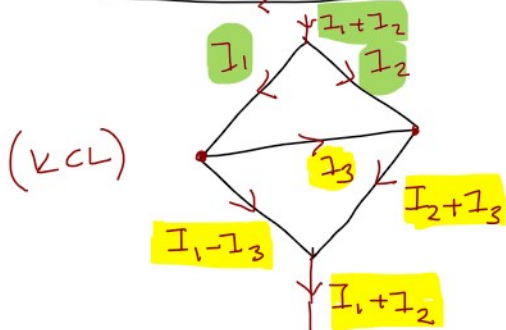

$$\textcircled{1} -I_1 - (I_1 - I_3) + 13 = 0$$

$$\textcircled{2} -I_2 - 2(I_2 + I_3) + 13 = 0$$

$$\textcircled{3} -I_2 + I_3 + I_1 = 0$$

$$\textcircled{1} \quad 13 = 2I_1 - I_3 \quad \Rightarrow \quad 13 = 2I_1 - I_3 \quad (\times 5)$$


$$\textcircled{2} \quad 13 = 3I_2 + 2I_3 \quad \Rightarrow \quad 13 = 3I_1 + 5I_3$$

$$\textcircled{3} \quad I_2 = I_1 + I_3 \quad + \quad \frac{13(6) = 13I_1}{I_1 = 6A}$$

$$I_2 = I_1 + I_3 = 6 - 1 = 5A$$


$$13 = 2(6) - I_3 \Rightarrow I_3 = -1A$$

R_{eq} of the circuit?

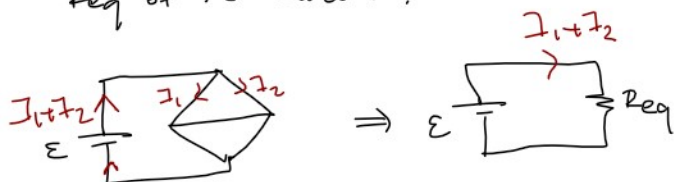


$$\mathcal{E} = (I_1 + I_2) R_{eq}$$



$$13 = (6 + 5) R_{eq}$$

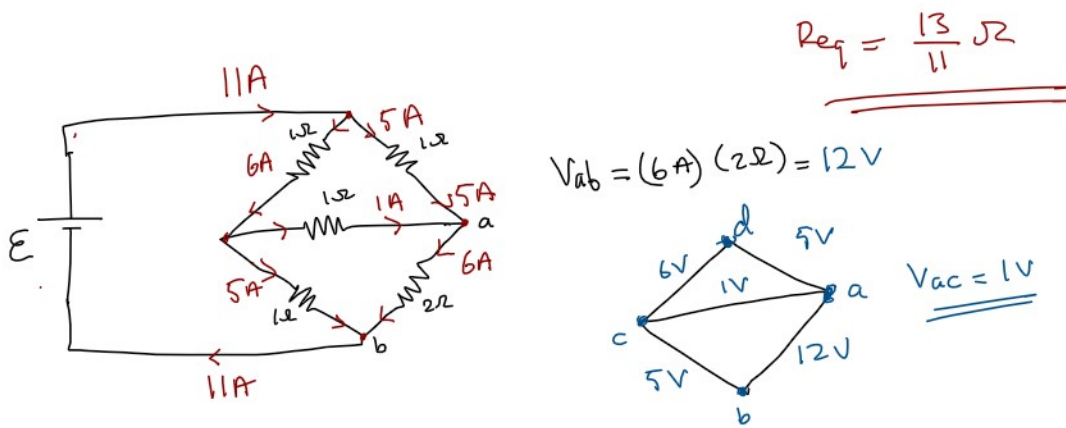


26.92)

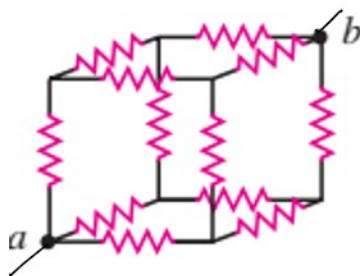

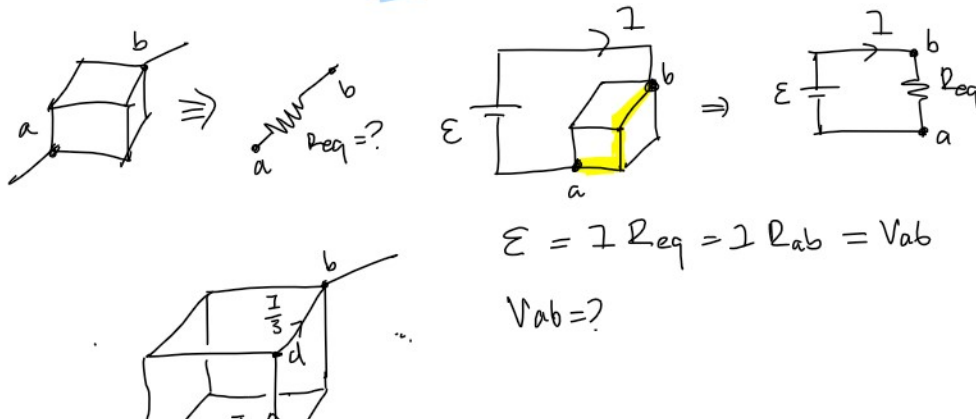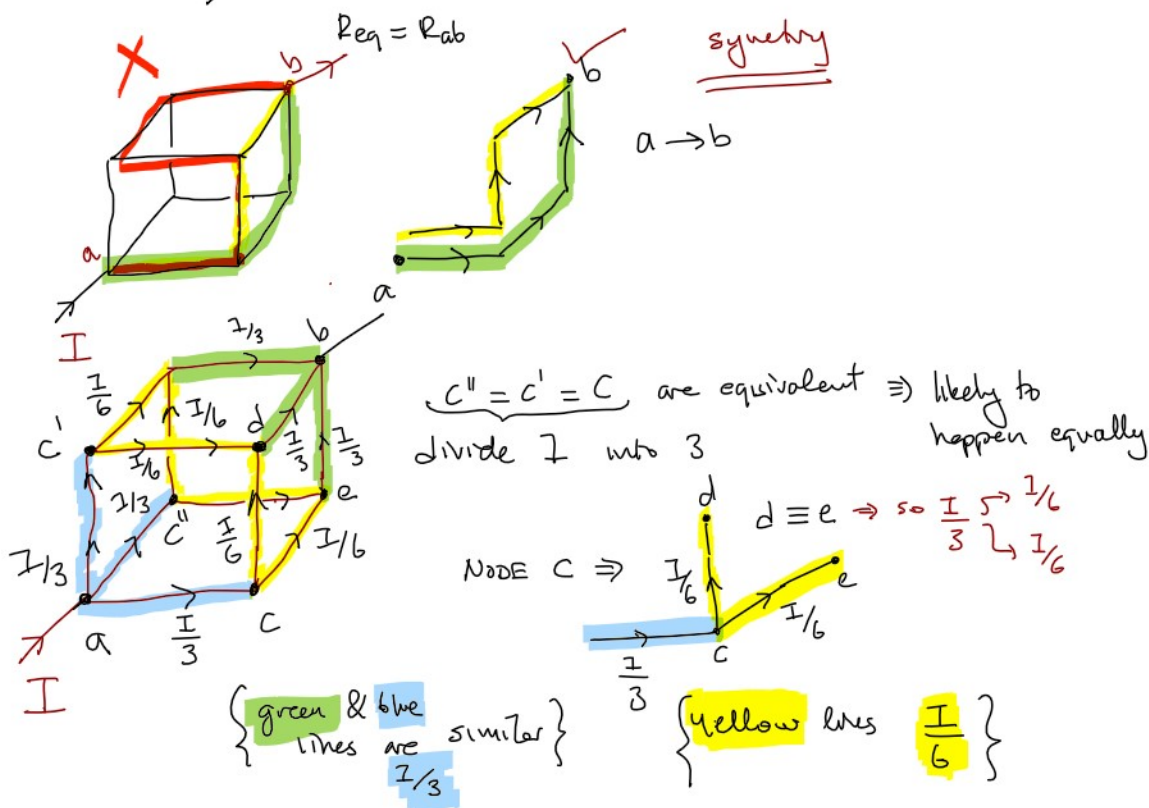26.92 ... Suppose a resistor R lies along each edge of a cube (12 resistors in all) with connections at the corners. Find the equivalent resistance between two diagonally opposite corners of the cube (points a and b in Fig. P26.92).



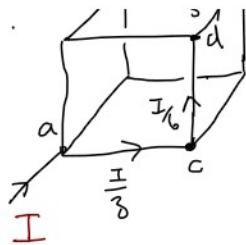


$$V_{ab} = V_{ac} + V_{cd} + V_{db}$$



$$V_{ab} = \frac{I}{3} R + \frac{I}{6} R + \frac{I}{3} R = I R_{ab}$$

$$R_{ab} = \frac{5}{6} R \quad \Leftarrow \quad \frac{5 I R}{6} = I R_{ab}$$


RC CIRCUITS

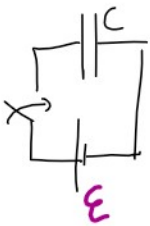

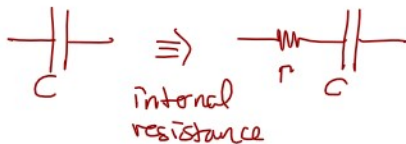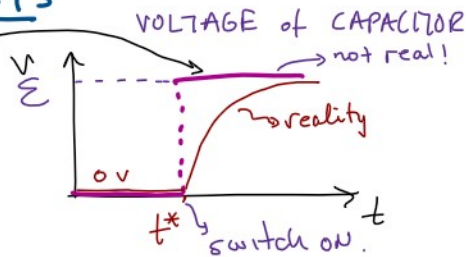When switch ON we thought capacitor FILLS UP immediately!




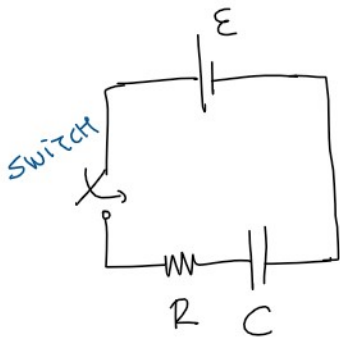even if we don't use external resistance capacitor always charged with RC circuit because capacitors have internal resistance




switch ON charges are running through towards the capacitor

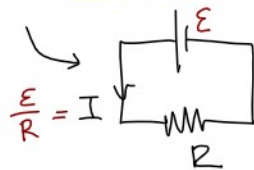$t = 0^+$ (very early times after switch is ON)



$I_{\max}$ (as if no capacitor!!)


$t \gg 0$ (very late stage)

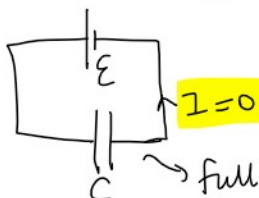

wait long enough; C is full
no current goes through R
(as if no resistor!!)

we will CHECK THESE with FORMULAS!
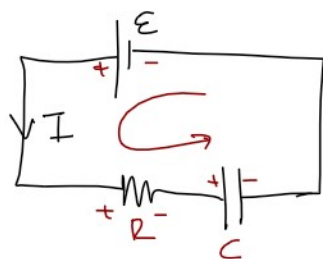
$$I \xrightarrow{\max} \frac{0}{\infty}$$



LET'S SOLVE for intermediate t times;

$$E - V_R - V_C = 0$$

$$E - IR - \frac{q}{C} = 0$$

$$I = \frac{dq}{dt}$$

$$C \frac{dq}{dt} = q - n \quad (\text{diff. eqn})$$

$$\tau = RC \quad \frac{dq}{dt} R - \frac{q}{C} = 0 \quad (\text{diff. eqn})$$

$$\frac{dq}{dt} = \left(\varepsilon - \frac{q}{C} \right) \frac{1}{R} \Rightarrow \frac{dq}{\left(\frac{\varepsilon C - q}{RC} \right)} = dt \Rightarrow \int \frac{dx}{x} = \ln x$$

$$\int \frac{dq}{\varepsilon C - q} = \int \frac{dt}{RC} \Rightarrow -\ln(\varepsilon C - q) \Big|_{q_i}^{q_f} = \frac{1}{RC} \Delta t \Big|_{t_i}^{t_f}$$

$$\ln(\varepsilon C - q_f) - \ln(\varepsilon C - q_i) = -\left(\frac{t_f - t_i}{RC} \right) \begin{cases} t_i = 0 \\ t_f = t \end{cases}$$


$$\ln(\varepsilon C - q(t)) - \ln(\varepsilon C) = -t/RC \quad \begin{cases} q_i = 0 \text{ (no charge at } t=0) \\ q_f = q(t) \end{cases}$$

$$\ln\left(\frac{\varepsilon C - q(t)}{\varepsilon C}\right) = -t/RC$$

$$\varepsilon C - q(t) = \varepsilon C e^{-t/RC} \Rightarrow q(t) = \varepsilon C - \varepsilon C e^{-t/RC}$$

$$q(t) = \varepsilon C (1 - e^{-t/RC})$$

CHARGE on the CAPACITOR at any time.

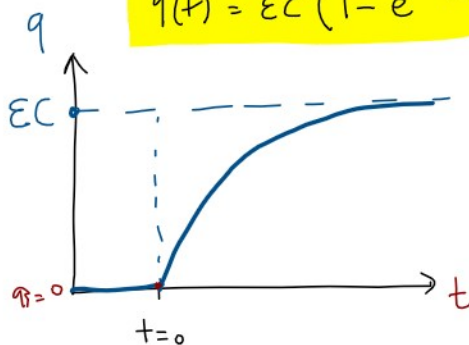


$$t=0 \quad q(0) = \varepsilon C (1 - e^0) = 0$$

$$t \rightarrow \infty \quad q(t \rightarrow \infty) = \varepsilon C (1 - e^{-\infty})$$

$$q = \varepsilon C (1 - e^{-t/RC}) = \varepsilon C (1 - 0) = \varepsilon C = q_{\max}$$

$$e^{-t/RC} = e^{-\left[\frac{s}{s} \right]} \quad \begin{matrix} \text{VF} \\ \text{no unit} \end{matrix}$$
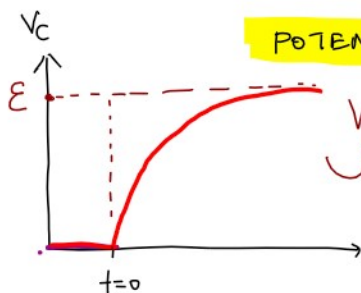
$$RC = [\text{second}]^* \quad [ZF = s]$$




POTENTIAL of the CAPACITOR

$$V_c = \frac{q(t)}{C} = \frac{\varepsilon C}{C} (1 - e^{-t/RC}) = \varepsilon (1 - e^{-t/RC}) = V_c$$

$$t=0 \quad V_c(t=0) = \varepsilon (1 - e^0) = \varepsilon (1 - 1) = 0$$

$$t \rightarrow \infty \quad V_c(t \rightarrow \infty) = \varepsilon (1 - e^{-\infty}) = \varepsilon (1 - 0) = \varepsilon$$

POTENTIAL of the RESISTOR

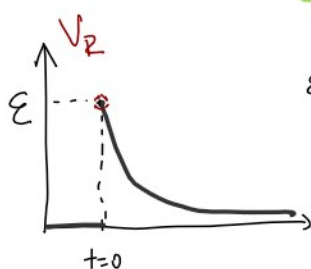

$$V_R = IR = \left(\frac{dq}{dt} \right) R$$

$$\varepsilon = V_c + V_R \Rightarrow V_R = \varepsilon - V_c = \varepsilon - (\varepsilon [1 - e^{-t/RC}])$$

$$V_R = +\varepsilon e^{-t/RC} = \frac{dq}{dt} R$$

$$t=0 \quad V_R(t=0) = \varepsilon e^0 = \varepsilon$$

$$t \rightarrow \infty \quad V_R(t \rightarrow \infty) = \varepsilon e^{-\infty} = 0$$


CURRENT on the CIRCUIT

CURRENT on the CIRCUIT

Since we know $q(t)$; $I = \frac{dq}{dt}$ (time derivative of charge)


$$I = \frac{d}{dt} (\epsilon C [1 - e^{-t/RC}]) = \epsilon C [0 - (-\frac{1}{RC}) e^{-t/RC}]$$
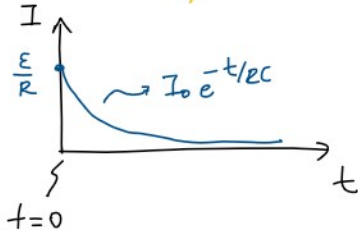
$$I = \frac{\epsilon C}{RC} e^{-t/RC} = \frac{\epsilon}{R} e^{-t/RC} = I_0 e^{-t/RC}$$



$$t=0 \quad I(t=0) = \frac{\epsilon}{R} e^{-0} = \frac{\epsilon}{R}$$
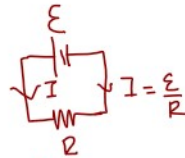
$$t \rightarrow \infty \quad I(t \rightarrow \infty) = \frac{\epsilon}{R} e^{-\infty} = 0$$



$$q = \epsilon C (1 - e^{-t/RC}) \quad \cancel{I(t)} = \frac{\epsilon}{R} e^{-t/RC} \quad V_R = IR \quad V_C = \frac{q}{C}$$

Dimensional analysis $[\epsilon C = VF = \text{Coulomb}]$

$$\left[\frac{\epsilon}{R} = \frac{V}{\Omega} = \frac{\text{second}}{\text{Ampere}} \right]$$

$$e^{-t/RC} = \text{unitless} \quad e^{-\left[\frac{s}{s}\right]} \quad RC = \text{seconds} \quad [SF = s]$$

$RC \equiv$ time const. of RC circuit $RC = \tau$ (tau)

$$q(t) = \epsilon C (1 - e^{-t/\tau}) \quad ; \quad I(t) = \frac{\epsilon}{R} e^{-t/\tau}$$

ex) $\epsilon = 12V \quad R = 100\Omega \quad C = 20\mu F \quad \tau = RC = 100(20) \times 10^{-6} s$
 $= 2000 \times 10^{-6} s$
 $= 2 \times 10^{-3} s = 2ms$

$$q(t) = (12V)(20\mu F) [1 - e^{-t/2ms}]$$



$$q(t) = 240\mu C [1 - e^{-t/2ms}]$$

@ $t = 1ms$ what's the charge on C?
 " " current of the circuit?

$$q(1ms) = 240\mu C [1 - e^{-1ms/2ms}] = 240\mu C [1 - \underbrace{e^{-1/2}}_{0.606}] = \underline{\underline{94.4\mu C}}$$

$$I(1ms) = ? \quad I = I_0 e^{-t/\tau} = \frac{\epsilon}{R} e^{-t/\tau} = \frac{240}{100} A e^{-1ms/2ms} = 2.4 e^{-1/2}$$
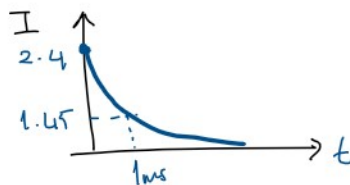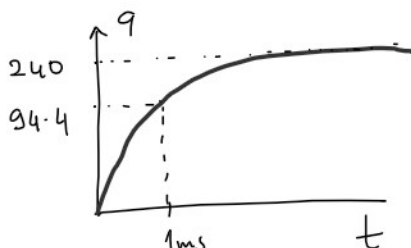
$$\underline{\underline{I(1ms) = 1.45A}}$$



$$q(t^*) = \frac{Q_{\max}}{2} = \epsilon C (1 - e^{-t^*/RC}) \Rightarrow \frac{\epsilon C}{2} = \epsilon C (1 - e^{-t^*/RC})$$

$$t^* = \text{time to fill half (0.50)} = T_{1/2}$$

$$\frac{1}{2} = 1 - e^{-t^*/RC}$$



$$e^{-t^*/RC} = \frac{1}{2}$$

$$-t^*/RC = \ln\left(\frac{1}{2}\right) = -0.69$$

$$\{0.69 (2\text{ms}) = 1.39\text{ms}\}$$

$$\Leftarrow t^* = 0.69 RC$$

DISCHARGING of CAPACITOR in RC circuit

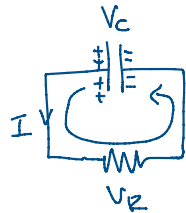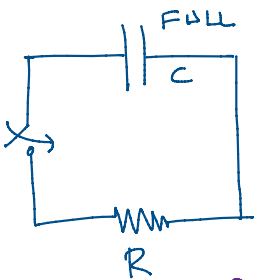

$$V_C - V_R = 0$$

$$\frac{q}{C} - IR = 0$$

$$\frac{q}{C} - \frac{dq}{dt} R = 0$$


$$\Leftarrow \frac{q}{C} = \frac{dq}{dt} R$$

$$\frac{t}{RC} = \frac{1}{RC} \Delta t \Big|_{t_i}^{t_f} = \ln q \Big|_{q_i=Q_0}^{q_f} = \ln q(t) - \ln Q_0$$



$$q(t) < Q_0$$

$$\ln \frac{q(t)}{Q_0} = -t/RC \quad \frac{q(t)}{Q_0} < 1 ; \ln(\dots) < 0$$


$$\ln \left| \frac{q(t)}{Q_0} \right| = -t/RC \Rightarrow \underline{q(t) = Q_0 e^{-t/RC}}$$

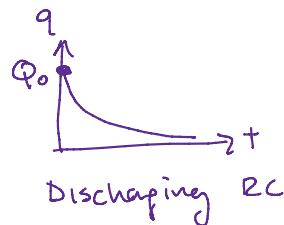
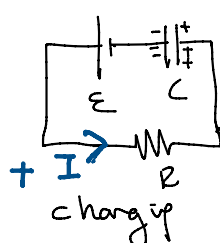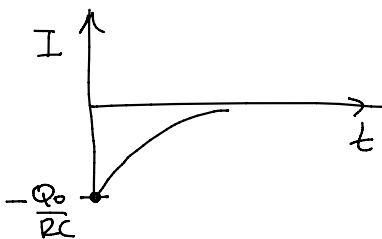
$$I = \frac{dq}{dt} = \left(-\frac{1}{RC}\right) Q_0 e^{-t/RC} = -\frac{Q_0}{RC} e^{-t/RC}$$



$\Rightarrow$

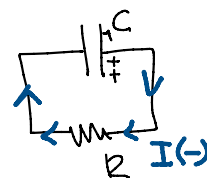


$$q(t) = Q_0 e^{-t/RC}$$

$$I = -\frac{Q_0}{RC} e^{-t/RC}$$

$$V_C = \frac{q}{C} = \frac{Q_0}{C} e^{-t/RC}$$


$$V_R = IR = -\frac{Q_0}{RC} e^{-t/RC} = -\frac{Q_0}{C} e^{-t/RC}$$
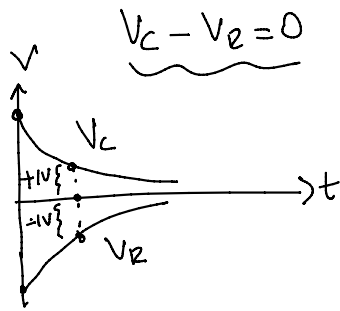
$$\checkmark \quad \underline{V_C - V_R = 0}$$




26.47 •• CP In the circuit shown in Fig. E26.47 each capacitor initially has a charge of magnitude 3.50 nC on its plates. After the switch S is closed, what will be the current in the circuit at the instant that the capacitors have lost 80.0% of their initial stored energy?

Figure **E26.47**

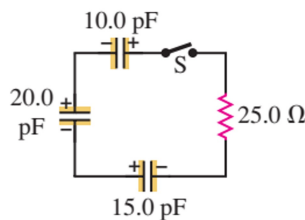

C_1, C_2, C_3
series
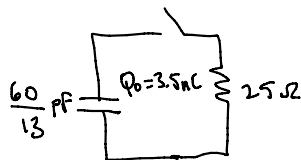
$$\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} = \frac{1}{C_{eq}} \Rightarrow \frac{1}{10} + \frac{1}{15} + \frac{1}{20} \Rightarrow \left(\frac{13}{60}\right)^{-1} = C_{eq} \quad 60/13 \text{ pF}$$



$$25 \frac{60}{13} \text{ pS} \approx 115 \text{ pS}$$

$$q(t) = Q_0 e^{-t/RC}$$

$$U = \frac{q^2}{2C} \rightarrow \text{lost 80\%}$$

$$q(t) = 3.5 \text{ nC} e^{-t/115 \text{ pS}}$$

$$I = ?$$

$$I(t) = \frac{-3.5 \text{ nC}}{115 \text{ pS}} e^{-t/115 \text{ pS}}$$

$$U = \frac{(3.5 \text{ nC})^2}{2 \left(\frac{60}{13}\right) \text{ pF}} = \frac{159.25}{120} \times \frac{(10^{-9})^2}{10^{-12}} = 1.3 \times 10^{-6} \text{ J} \Rightarrow \frac{20}{100} \quad 1.3 \times 10^{-6}$$

$$\frac{U_f}{U_i} = \frac{20}{100} = \frac{(q_f^2)/2C}{(q_i^2)/2C} \Rightarrow q_f = \sqrt{0.2 q_i^2} = \sqrt{0.2} (3.5 \text{ nC})$$

$$q(t) = 3.5 \text{ nC} e^{-t/115 \text{ pS}} = \sqrt{0.2} 3.5 \text{ nC} \Rightarrow e^{-t/115 \text{ pS}} = \sqrt{0.2}$$



$$t = -\ln(\sqrt{0.2}) 115 \text{ pS}$$

$$-(-0.8) 115 \text{ pS} = 92 \text{ pS}$$

$$I(t=0.92 \text{ pS}) = \frac{-Q_0}{RC} e^{-t/RC} \Rightarrow 115$$

$$- \frac{3.5 \text{ nC}}{115 \text{ pS}} e^{-92/115} = \checkmark$$

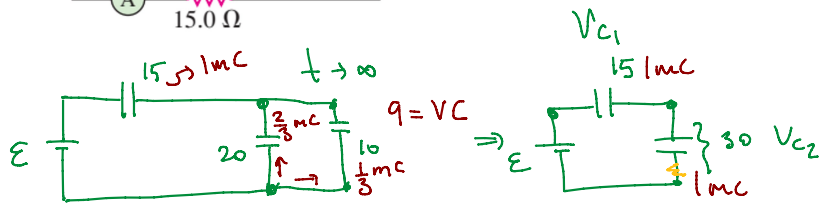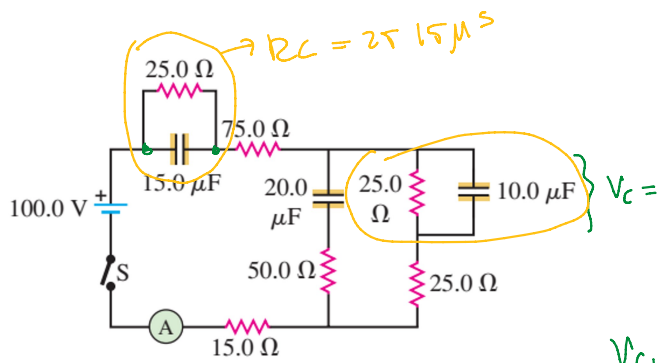$25.0 \Omega \rightarrow RC = 25.15 \mu\text{s}$



$$V_{C1} + V_{C2} = \varepsilon$$

$$\frac{q}{C_1} + \frac{q}{C_2} = \varepsilon = \frac{q}{C_{eq}}$$

$$C_{eq} = \frac{15(30)}{45} = 10 \mu F$$

$$q = \varepsilon C_{eq}$$

$$= (100 \text{ V}) 10 \mu F$$

$$= 1000 \mu C = 1 \text{ mC}$$

$$q_0 e^{-t/RC}$$

$$q_0 (1 - e^{-t/RC})$$

